

## Operation of FET:

In JFET, the p-n junction b/w gate and source is always kept in reverse biased conditions, since the current in a reverse biased p-n junction is extremely small, practically zero.

From fig(a) the voltage  $V_{DD}$  is applied b/w drain and source. Gate terminal is kept open, due to polarities of applied voltage.

$V_{DD}$  on the majority carriers i.e., the electrons start flowing

Scanned with CamScanner


 



fig 5.1 n-channel JFET with gate open

from source to drain. this flow of electrons makes the drain current,  $I_D$ . the majority charge carriers moves from source to drain through the space b/w the gate regions. the space is commonly known as channel. the width of this channel can be controlled by varying the gate voltage. To see the effect of gate voltage on channel width and on drain current  $I_D$ ,


consider the diagram shown below

 

(a) No bias voltage on gate

 

(b) small negative gate-source bias

 

(c) Large negative gate-source bias

fig(a) shows that an n-channel JFET with gate directly connected to the source terminal, when drain voltage is applied ( $V_{DS}$ ), a drain current  $I_D$  flows in the direction shown. since the n-material is resistive, the drain current causes the voltage drop along the channel. Since gate is heavily doped & the channel is lightly doped, the width of the depletion region will spread in the channel. This penetration depends on the reverse bias voltage.

The depletion width across drain is more than the source because the voltage at drain side is more than voltage at the source. The depletion region does not have charge carriers, the space b/w

The depletion width across drain is more than the source because the voltage at drain side is more than voltage at the source side. The depletion region does not have charge carriers, the space b/w two depletion regions is available for the conduction of channel. If we extremely applied reverse bias voltage to the gate, the

Scanned with CamScanner

reverse bias will further increases and hence increases the depletion region which reduces the conducting portion of the channel.

As width of the conducting portion of the channel reduces, the no of electrons flowing from source to drain reduces and hence the current flowing from drain to source reduces.

If we go on increasing the reverse bias voltage to gate as shown in fig (b) and (c), the depletion regions will increase more and more, and stage will come when the width of depletion region will be equal to the original width of the channel shown in fig (c). This will prevent current flow from drain to source and this will cutoff the drain current. The gate to source voltage that produces cutoff is known as "cut-off voltage" and denoted by  $V_{GS(off)}$ .

When the gate is shorted to source (fig (a)), there is minimum reverse bias b/w gate and source p-n junction, making depletion region width minimum and conducting channel width is maximum. In this case maximum possible drain current flows which is design-ated by  $I_{DSS}$ . It is clear that the gate to source voltage controls the current flowing through the channel and FET is also called "voltage controlled current source".

Transfer characteristics for n-channel JFET:

For transfer characteristics keep  $V_{DS}$  as constant by varying  $V_{GS}$ , note down corresponding values of  $V_{GS}$  and  $I_D$

$V_{DS} = \text{constant}$			
$V_{GS}$ vary	$V_{GS}$	$I_D$	

Scanned with CamScanner

### Transfer characteristics for p-channel JFET:

The transfer characteristics of p-channel JFET is identical to transfer characteristics of n-channel JFET except that the polarities of  $V_{GS}$  and  $I_D$  are reversed.


 
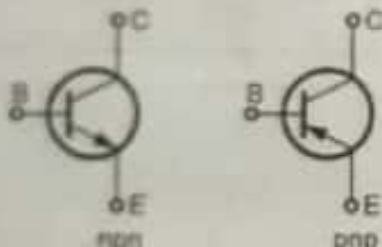


fig: Transfer characteristics of p-channel JFET

## 7.9 Comparison of BJT and FET

Sr. No.	Parameter	BJT	FET
1.	Control element	Current controlled device. Input current $I_B$ controls output current $I_C$ .	Voltage controlled device. Input voltage $V_{GS}$ controls drain current $I_D$ .
2.	Device type	Current flows due to both, majority and minority carriers and hence bipolar device.	Current flows only due to majority carriers and hence unipolar device.
3.	Types	n-p-n and p-n-p	n-channel and p-channel.
4.	Symbols		
5.	Configurations	CE, CB, CC	CS, CG, CD
6.	Input resistance	Less compare to JFET.	High compare to BJT.
7.	Size	Bigger than JFET.	Smaller in construction than BJT, thus making them useful in integrated-circuits (IC).

8	Sensitivity	Higher sensitivity to changes in the applied signals.	Less sensitivity to changes in the applied voltage.
8	Thermal stability	Less	More
10	Thermal runaway	Exists in BJT, because of cumulative effect of increase in $I_C$ with temperature, resulting increase in temperature in the device.	Does not exist in JFET, because drain resistance $r_d$ increases with temperature, which reduces $I_D$ reducing the $I_D$ and hence the temperature of the device.
11	Relation between input and output	Linear	Non-linear
12	Ratio of o/p to i/p	$\frac{\Delta I_C}{\Delta I_B} = \beta$	$\frac{\Delta I_D}{\Delta V_{GS}} = g_m$
13	Thermal noise	More in BJT as more charge carriers cross junctions.	Much lower in JFET as very few charge carriers cross the junction.
14	Gain bandwidth product	High	Low

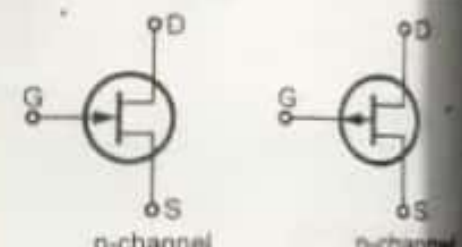

## 2) B) Relation b/w $\mu$ , $r_d$ and $g_m$ :-

### JFET parameters :-

#### Transconductance ( $g_m$ )

It is defined as change in drain current for a change in gate source with constant drain to source voltage.

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \Big|_{V_{DS} \text{ constant}}$$

Transconductance is also called mutual conductance

#### Drain to Source Resistance :-

Drain resistance ( $r_d$ ) is the AC resistance b/w drain and source terminals when JFET is operating in saturation region.

$$r_d = \frac{\Delta V_{DS}}{\Delta I_D} \Big|_{V_{GS} \text{ constant}}$$



Amplification factor ( $\mu$ ) :-

It is defined as change in drain to source terminals for change in gate source with constant drain current.

$$\mu = \left. \frac{\Delta V_{DS}}{\Delta V_{GS}} \right|_{I_D \text{ constant}}$$

$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS} \text{ constant}}$$

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} \text{ constant}}$$

$$\mu = \left. \frac{\Delta V_{DS}}{\Delta V_{GS}} \right|_{I_D \text{ constant}}$$


$$\therefore \mu = r_d \times g_m$$

$$\frac{\Delta V_{DS}}{\Delta V_{GS}} = \frac{\Delta V_{DS}}{\cancel{\Delta I_D}} \times \frac{\cancel{\Delta I_D}}{\Delta V_{GS}}$$

$$\frac{\Delta V_{DS}}{\Delta V_{GS}} = \frac{\Delta V_{DS}}{\Delta V_{GS}}$$



## → characteristics of tunnel diode.

 

The tunnel diode exhibits a negative resistance characteristic between peak current  $I_p$  and valley current  $I_v$ .

The tunnel diode is excellent conductor in forward bias conditions.



By applying small forward bias voltage to the tunnel diode the current increases and reaches to maximum level. The maximum current for small forward bias voltage is called as "peak current" ( $I_p$ ). The corresponding voltage to the peak current is called "peak voltage" ( $V_p$ ).

Scanned with CamScanner

→ If the forward bias voltage is increased beyond the peak voltage the current starts decreasing and reaches to minimum level. This minimum value of current is called as "valley current" ( $I_v$ ). The corresponding voltage to valley current is called as "valley voltage" ( $V_v$ ).

If forward bias voltage is increased beyond valley voltage it exhibits the same characteristics as ordinary diode.

  
The symbol and equivalent circuit of tunnel diode is shown below:



Scanned with CamScanner

## → UJT characteristics

The characteristic curve between

 

Here, upto the peak point ( $V_p$ ), the diode is reverse biased and hence, the region to the left of the peak point is called cut-off region.

At peak point, the peak voltage

$$V_p = \eta V_{BB} + V_0$$

The diode starts conduction + holes are injected into n-layer. Hence, resistance decreases thereby decreasing  $V_E$  for the increase in  $I_E$ . So, there is a negative neg resistance region from peak point  $V_p$  to valley point  $V_v$ .


After the valley point, the device is driven into saturation and behaves like a conventional forward biased pn junction diode. The region to the right of the valley point is called saturation region.

In the valley point, the resistance changes from negative to positive and it remains positive in saturation region.

Due to the negative resistance property, a UJT can be employed in a variety of applications, viz a sawtooth wave generator, pulse generator etc.

on characteristics.

 The characteristics of an SCR are shown for various values of current.



#### 1. Forward breakdown voltage, $V_{(BR)F*}$

It is that voltage above which the SCR enters the conduction region.

The asterisk (\*) is a letter that is to be added that is dependent on the condition of the gate terminal as follows:

- O = open circuit from G to K
- S = short circuit from G to K
- R = resistor from G to K
- V = fixed bias-voltage from G to K.

#### 2. Holding current, $I_H$

It is that current value below which the SCR switches from the conduction state to forward blocking region under stated conditions.

#### 3. Forward & Reverse blocking regions

These are the regions corresponding to the open circuit condition for the controller rectifier which block the flow of charge (current) from anode to cathode.

#### 4. Reverse breakdown voltage

It is equivalent to the zone of avalanche region of the fundamental two-layer semiconductor diode.

SCR characteristics are very similar to those of the basic 2-layer semiconductor diode except for the horizontal offset before entering the conduction region. It is this horizontal jutting region that gives the gate control over the response of SCR.

For  $I_G = 0$ ,  $V_F$  must reach the largest required breakdown voltage ( $V_{(BR)F*}$ ) before the "collapsing" effect will result and the SCR can enter the conduction region corresponding to the "on" state.

If the gate current is increased to  $I_{G1}$ , by applying a bias voltage to the gate terminal, the value of  $V_F$  required for the conduction ( $V_{F1}$ ) is considerably less. The holding current  $I_H$  also drops with increase in  $I_G$ .

If the gate current is further increased to  $I_{G2}$ , the SCR will fire at very low values of voltage ( $V_{F3}$ ) and the characteristics begin to approach those of the basic pn junction diode.



1. Why thermal runaway is not there in FETs ?

## 8.2 Biasing Circuits for FET

Different biasing circuits of FET are :

- Fixed bias circuit
- Self bias circuit
- Voltage divider bias circuit

### 8.2.1 Fixed-bias Circuit

Fig. 8.2.1 shows the fixed bias circuit for the n-channel JFET. This is the simplest biasing arrangement. To make gate-source junction reverse-biased, a separate supply  $V_{GG}$  is connected such that gate is more negative than the source.

 


Fig. 8.2.1 Fixed bias circuit for n-channel circuit

 


Fig. 8.2.2 Simplified fixed bias circuit

For the d.c. analysis coupling capacitors are open circuits. The current through  $R_G$  is zero. This permits  $R_G$  to be replaced by a short circuit equivalent, simplifying the circuit as shown in the Fig. 8.2.2.

Step 1: Calculate  $V_{GS}$

For d.c. analysis  $I_G = 0$  A and applying KVL to the input circuit we get,

$$V_{GS} + V_{GG} = 0$$

$$V_{GS} = -V_{GG}$$

Since  $V_{GG}$  is a fixed d.c. supply, the voltage  $V_{GS}$  is fixed in magnitude, and hence the fixed bias circuit. ... (8.2.1)

Step 2: Calculate  $I_{DQ}$

The drain current  $I_D$  can be calculated using equation,

$$I_{DQ} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

Step 3: Calculate  $V_{DS}$

The drain to source voltage of drain circuit can be determined by applying KVL.

$$V_{DD} - I_D R_D - V_{DSQ} = 0$$

$$V_{DSQ} = V_{DD} - I_D R_D \quad \dots (8.2.2)$$

The main drawback of fixed bias circuit of FET is that it requires two power supplies.

### 8.2.2 Voltage Divider Bias Circuit

The Fig. 8.2.4 shows n-channel JFET with voltage divider bias. The voltage at the source of the JFET must be more positive than the voltage at the gate in order to keep the gate-source junction reverse-biased. The source voltage is,

$$V_S = I_D R_S$$

The gate voltage is set by resistors  $R_1$  and  $R_2$ . Coupling capacitors  $C_1$  and  $C_2$  and source resistor bypass capacitor  $C_S$  are assumed to be open circuit for DC analysis.

 


Fig. 8.2.4 Voltage divider bias for n-channel JFET

**D.C. analysis :**

**Step 1 :** Calculate  $V_G$

$$V_G = \frac{V_{DD} R_2}{R_1 + R_2} \quad \because I_G = 0$$

**Step 2 :** Obtain expression for  $V_{GS}$

Applying KVL to the input circuit we get,

$$V_G - V_{GS} - I_D R_S = 0$$

$$\therefore V_{GS} = V_G - I_D R_S \quad \dots (8.2.3)$$

**Step 3 :** Calculate  $I_{DQ}$

The  $I_{DQ}$  can be calculated using equation :

$$I_{DQ} = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

**Step 4 :** Calculate  $V_{DS}$  and  $V_{GS}$

Applying KVL to the output circuit we get,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

 


Fig. 8.2.5 Simplified voltage divider circuit for d.c. analysis



$$\begin{aligned}\therefore V_{DS} &= V_{DD} - I_D R_D - I_D R_S \\ &= V_{DD} - I_D (R_D + R_S) \quad \dots (8.2.4)\end{aligned}$$

The Q point of a JFET amplifier using the voltage divider bias is given by :


$$I_{DQ} = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$V_{DSQ} = V_{DD} - I_D (R_D + R_S)$$

$$V_{GSQ} = V_G - I_D R_S$$
 
## 8.2.3 Self Bias Circuit

Self bias is the most common type of JFET bias. Recall that a JFET must be operated such that the gate source junction is always reverse-biased. This condition requires a negative  $V_{GS}$  for an n-channel JFET and a positive  $V_{GS}$  for p-channel JFET. This can be achieved using the self bias arrangement shown in Fig. 8.2.10. The gate resistor,  $R_G$ , does not affect the bias because it has essentially no voltage drop across it; and therefore the gate remains at 0 V.  $R_G$  is necessary only to isolate an a.c. signal from ground in amplifier applications. The voltage drop across resistor,  $R_S$ , makes gate source junction reverse biased.



Note :  $I_S = I_D$  in all JFETs

Fig. 8.2.10 Self bias circuits for JFET

### D.C. analysis :

#### Step 1 : Obtain expression for $V_{GS}$

For the n-channel FET in Fig. 8.2.10 (a),  $I_S$  produces a voltage drop across  $R_S$  and makes the source positive with respect to ground. Since  $I_S = I_D$  and  $V_G = 0$ , then

$V_S = I_S R_S = I_D R_S$ . The gate to source voltage is,

$$V_{GS} = V_G - V_S = 0 - I_D R_S = -I_D R_S$$

For the p-channel FET in Fig. 8.2.10 (b),  $I_S$  produces a voltage drop across  $R_S$  and makes the source negative with respect to ground. Since  $I_S = I_D$  and  $V_G = 0$ , then

$$V_S = -I_S R_S = -I_D R_S. \text{ The gate to source voltage is}$$

$$V_{GS} = V_G - V_S = 0 - (-I_D R_S) = +I_D R_S$$

In the following d.c. analysis, the n-channel JFET shown in Fig. 8.2.10 (a) is used to for illustration. For d.c. analysis we can replace coupling capacitors by open circuits and we can also replace the resistor  $R_G$  by a short circuit equivalent, since  $I_G = 0$ . This is illustrated in Fig. 8.2.11.

**Step 2 :** Calculate  $I_{DQ}$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

Substituting value of  $V_{GS}$  in above equation we get,


$$I_D = I_{DSS} \left( 1 - \frac{-I_D R_S}{V_p} \right)^2 = I_{DSS} \left( 1 + \frac{I_D R_S}{V_p} \right)^2 \quad \dots (8.25)$$

**Step 3 :** Calculate  $V_{DS}$

Applying KVL to the output circuit we get,

$$V_S + V_{DS} + I_D R_D - V_{DD} = 0$$

$$\therefore V_{DS} = V_{DD} - V_S - I_D R_D = V_{DD} - I_D R_S - I_D R_D = V_{DD} - I_D (R_S + R_D)$$

 

**Fig. 8.2.11** Simplified self bias circuit for d.c. analysis



**Q35. Discuss Zener and avalanche breakdown mechanisms.**

**Ans:**

The diode enters the breakdown region when the magnitude of the reverse voltage exceeds a threshold value that is specific to the particular diode, called the breakdown voltage. In the breakdown region for very small variation in voltage the current increases rapidly. There are two types of breakdown mechanisms,

1. Avalanche breakdown
2. Zener breakdown.

1. **Avalanche Breakdown:** In this mechanism thermally generated electron-hole pairs gain energy from the external voltage applied and break the covalent bonds to produce new electron-hole pairs. These new electron-hole pairs, in turn, generate more electron-hole pairs by disrupting bonds and the process continues cumulatively. This cumulative process is known as Avalanche Multiplication. Due to this large current is seen at the terminals of diodes for small variations in voltage.
2. **Zener Breakdown:** In this mechanism electron-hole pairs are generated by applying strong electric field. Because of the presence of strong electric field direct rupture of covalent bonds takes place. Due to this new electron-hole pairs are generated. The breakdown occurring due to application of strong electric fields is known as Zener breakdown.

**Q36.** With neat diagram, explain the operation of Zener diode and its forward and reverse characteristics. Also distinguish between Avalanche and Zener Break downs.

**Ana:**

**Zener Diode:** The power dissipated at the junction of a normal PN diode operating in breakdown region is very large. Due to large power dissipation, the diode gets damaged. The diode which is designed to operate in breakdown region under certain conditions is known as Zener diode. Zener diode is heavily doped than normal PN-Junction diodes. The circuit symbol of Zener diode is as shown in figure (1).

**Characteristics:** Figure (2) illustrates that V-I characteristics of Zener diode.

 


Figure (1): Symbol of Zener Diode

 


Figure (2): V-I Characteristics of Zener Diode

It can be observed from figure (2) that under forward biased condition, a zener diode operates like an ordinary diode. Under reverse-biased condition, an increase in reverse voltage ( $V_r$ ), decreases the reverse current ( $I_r$ ). A further increase in  $V_r$  causes a sharp breakdown in  $I_r$ . Such breakdown in zener diode is called zener breakdown and the voltage at which breakdown occurs is called zener voltage ( $V_z$ ). After, the breakdown, zener diode operates with a constant voltage.

The breakdown in voltage largely depends on the amount of doping. If the diode is heavily doped, the width of depletion layer decreases and the breakdown occurs at a lower reverse voltage. On the other hand, if diode is lightly doped, a higher breakdown of voltage occurs.

Look for the **SIA GROUP LOGO** on the **TITLE COVER** before you buy