

Figure (2)

**Q35. Mention the applications of a differentiator and integrator circuit.**

**Ans:**

#### Applications of Differentiator

Differentiator (or) High pass RC circuit finds its applications in,


- (i) Wave shaping circuits (such as conversion of pulses into spikes).
- (ii) FM demodulator.

#### Applications of Integrator

Integrator circuits (or) low pass RC circuits are widely used in,

- (i) Analog computers
- (ii) Analog to digital computers
- (iii) Wave shaping circuits (such as conversion of square waves into triangular waves)
- (iv) Filter
- (v) Ramp generators
- (vi) Servo control system.

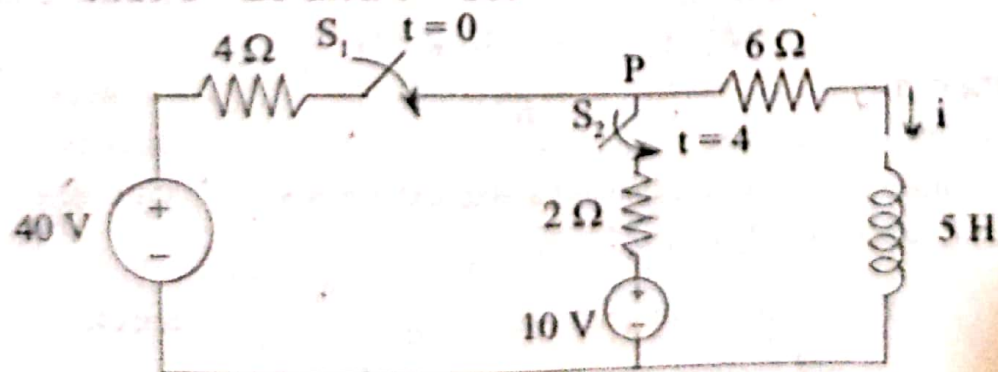**Q36. At  $t = 0$ , switch 1 in figure is closed, and switch 2 is closed 4s later. Find  $i(t)$  for  $t > 0$ . Calculate  $i$  for  $t = 2s$  and  $t = 5s$ .**




Figure



Ans:

The given circuit is shown in figure,

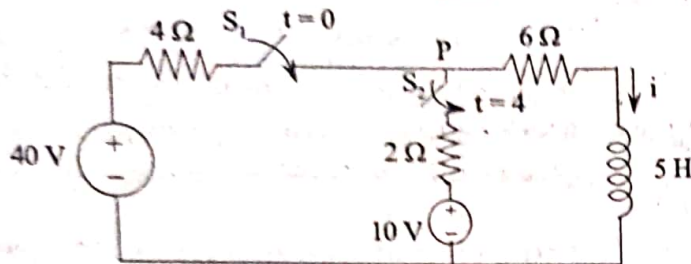

Figure

To determine,

$i(t)$  for  $t > 0$  and

$i(t)$  for  $t = 2s$  and  $t = 5s$

In order to find  $i(t)$  considering three time intervals i.e.,  $t \leq 0$ ,  $0 \leq t \leq 4$  and  $t \geq 4$  separately. The switches  $S_1$  and  $S_2$  are opened for  $t < 0$  and current through the inductor is zero i.e.,  $i = 0$ , because inductor doesn't allow the sudden changes in current.

Thus,

$$i(0^-) = i(0) = i(0^+) = 0$$

For  $0 \leq t \leq 4$ , switch  $S_1$  is closed and  $S_2$  is still open.

Then,

$$i(\infty) = \frac{40}{4+6} = \frac{40}{10}$$

$$\therefore i(\infty) = 4 \text{ A}$$

Now,

Equivalent resistance,  $R = 4 + 6 = 10 \Omega$

Time constant,  $\tau = \frac{L}{R}$

$$\tau = \frac{5}{10} = \frac{1}{2} \text{ s} = 0.5 \text{ s}$$

Thus,

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$= 4 + [0 - 4]e^{-t/0.5}$$

$$= 4 - 4e^{-2t}$$

$$\therefore i(t) = 4(1 - e^{-2t}) \text{ A}, \quad 0 \leq t \leq 4$$

For  $t \leq 4$ , switch  $S_2$  is closed. Since the inductor doesn't allow the sudden changes in current, the initial current at  $t = 4$  is,

$$i(4) = i(4^-) = 4(1 - e^{-2(4)})$$

$$= 4(1 - e^{-8})$$

$$= 4(1 - 3.35 \times 10^{-4})$$

$$= 4(0.99)$$

$$i(4) = 3.96 \approx 4$$

$$\therefore i(4) = 4 \text{ A}$$

To find  $i(\infty)$ , assume the voltage ' $V$ ' at node  $P$ . Now, applying KCL at node  $P$ , we get,

$$\frac{40 - V}{4} + \frac{10 - V}{2} = \frac{V}{6}$$

$$V \left( \frac{1}{6} + \frac{1}{4} + \frac{1}{2} \right) = \frac{40}{4} + \frac{10}{2}$$

$$V \left( \frac{2+3+6}{12} \right) = 10 + 5$$

$$V \left( \frac{11}{12} \right) = 15$$

$$\therefore V = \frac{180}{11} = 16.363 \text{ V}$$

Thus,

$$i(\infty) = \frac{V}{6} = \frac{16.363}{6}$$

$$i(\infty) = 2.727 \text{ A}$$

At the inductor terminal, the equivalent resistance is,

$$R = 4 \parallel 2 + 6$$

$$= \frac{4 \times 2}{4 + 2} + 6$$

$$= \frac{8}{6} + 6 = \frac{8 + 36}{6} = \frac{44}{6}$$

$$R = \frac{22}{3} \Omega = 7.333 \Omega$$

And,

$$\tau = \frac{L}{R} = \frac{5}{7.333} = 0.6818 \text{ s}$$

Hence,

$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-(t-4)/\tau}, \quad t \geq 4$$

The term  $(t - 4)$  in the exponential is due to time delay. Thus, substituting  $i(\infty)$ ,  $i(4)$  and  $\tau$  values in the above equation, we get,

$$i(t) = 2.727 + [4 - 2.727]e^{-(t-4)/0.6818}$$

$$= 2.727 + [1.273]e^{-(t-4)(1.466)}$$

$$\therefore i(t) = 2.727 + 1.273e^{-(t-4)(1.466)}, \quad t \geq 4$$

Hence,

$$i(t) = \begin{cases} 0, & t \leq 0 \\ 4(1 - e^{-2t}), & 0 \leq t \leq 4 \\ 2.727 + 1.273e^{-1.466(t-4)}, & t \geq 4 \end{cases}$$



Now,

At  $t = 2s$ ,

$$\begin{aligned} i(2) &= 4(1 - e^{-2(2)}) \\ &= 4(1 - e^{-4}) \\ &= 4(1 - 0.0183) \\ &= 4(0.98) \end{aligned}$$


$$\therefore i(2) = 3.92 \text{ A}$$

At  $t = 5s$ ,

$$\begin{aligned} i(5) &= 2.727 + 1.273e^{-1.466(5-4)} \\ &= 2.727 + 1.273e^{-1.466} \\ &= 2.727 + 1.273(0.2308) \\ &= 2.727 + 0.293 \end{aligned}$$

$$\therefore i(5) = 3.020 \text{ A}$$

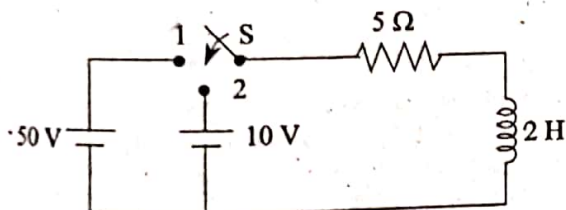
Q37. In the circuit as shown in figure, the switch S is in position 1 for a long time and brought the position 2 at time  $t = 0$ . Determine the circuit current.



Figure

Ans:

The given circuit is shown in figure,

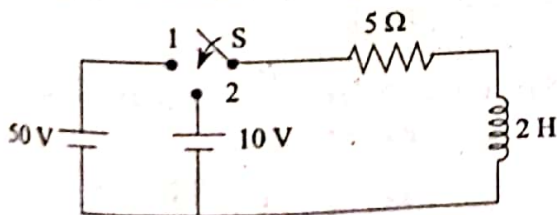

Figure

Let, current  $i$  be flowing through the circuit when the switches are close.

In figure, switch 'S' is at position-1 for steady state condition.

At,  $t = 0$ .

$\therefore$  Current through the inductor is given as,

$$\begin{aligned} i &= \frac{V_1}{R} \\ &= \frac{50}{5} = 10 \text{ A} \end{aligned}$$

The inductor will not allow to change the current through it.

$$\therefore i(0^-) = i(0^+) = 10 \text{ A}$$

It is required to obtain the current response after the switch is moved to position 2.

$\therefore$  The current in the circuit is,

$$i(t) = c_1 + c_2 e^{-\frac{R}{L}t} \quad \dots (1)$$

We know that,

$$\text{At } t = 0, i = 10 \text{ A}$$

Substituting the values in equation (1),

$$\Rightarrow 10 = c_1 + c_2 e_0$$

$$\Rightarrow c_1 + c_2 = 10 \quad \dots (2)$$

Now, switch is moved to position 2 i.e., at  $t = \infty$

$$\begin{aligned} i &= \frac{V_2}{R} \\ &= \frac{10}{5} = 2 \text{ A} \end{aligned}$$

Substituting the values in equation (1), we have,

$$\begin{aligned} 2 &= c_1 + c_2(0) \\ c_1 &= 2 \end{aligned}$$

Substituting  $c_1$  in equation (2), we get,

$$\begin{aligned} c_1 + c_2 &= 10 \\ c_2 &= 10 - 2 \\ c_2 &= 8 \end{aligned}$$

$\therefore$  The current in the circuit is,

$$\begin{aligned} i(t) &= 2 + 8e^{-\frac{5}{2}t} \\ &= 2(1 + 4e^{-2.5t}) \end{aligned}$$

Q38. A symmetrical square wave whose peak-to-peak amplitude is 2 V and whose average value is zero as applied to an RC integrating circuit. The time constant is equal to half period of the square wave. Find the peak-to-peak value of the output amplitude.

Ans: Given that,

Peak-to-peak amplitude of symmetrical square wave,  $V = 2$  Volts

Time constant is equal to half the time period of the square wave.

$$\Rightarrow RC = \frac{T}{2}$$

**Peak-to-peak Value of the Output Amplitude:** Since, it is given that a symmetrical square wave with zero average value is applied to an RC integrating circuit (i.e., low-pass circuit), the output waveform will also be symmetrical. The positive and negative peaks in the output waveform will be equal in magnitude but opposite in direction. The output waveform is shown in figure.

Here,  $V_1 = -V_2$

We know that in an RC integrating circuit, when a symmetrical square wave is applied,  $V_1$  is given by,

$$V_1 = \frac{V}{2} \left[ \frac{1 - e^{-T/2RC}}{1 + e^{-T/2RC}} \right]$$

Substituting the given values, we get,


$$\Rightarrow V_1 = \frac{2}{2} \left[ \frac{1 - e^{-\frac{-T}{2} \cdot \frac{2}{T}}}{1 + e^{-\frac{-T}{2} \cdot \frac{2}{T}}} \right]$$

$$\Rightarrow V_1 = \left[ \frac{1 - e^{-1}}{1 + e^{-1}} \right]$$

$$\Rightarrow V_1 = \frac{0.632}{1.368}$$

$$\Rightarrow V_1 = 0.4621$$
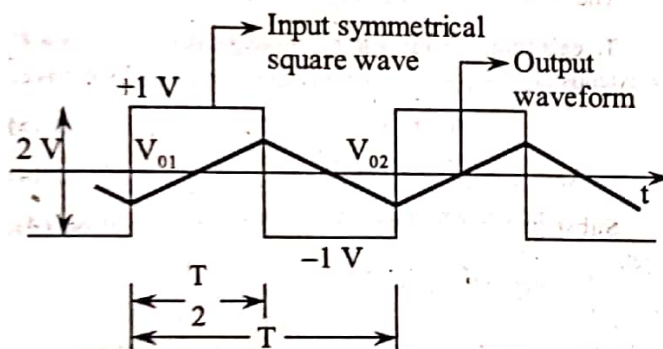
$$\therefore V_2 = -V_1 = -0.4621 \text{ Volts}$$



Figure

So, peak-to-peak value of the output amplitude varies from  $-0.4621 \text{ V}$  to  $0.4621 \text{ V}$ .

$$\text{Peak-to-peak amplitude} = 0.4621 - (-0.4621) = 0.9242 \text{ V}$$

$$\therefore \text{Peak-to-peak amplitude} = 0.924 \text{ V}$$

**Q39.** An RC differentiator circuit is driven from a 500 Hz symmetrical square wave of 10 V peak-to-peak. Calculate the output voltage levels under steady state if  $RC = 1 \text{ msec}$ .

**Ans:** Given that,

For an RC differentiator circuit,

Peak-to-peak amplitude of input square wave,

$$V = 10 \text{ volts}$$

$$\text{Time constant, } \tau = RC = 1 \text{ msec}$$

Frequency of symmetrical square wave,  $f = 500 \text{ Hz}$

The square wave applied at the input of differentiator is

shown in figure (1).

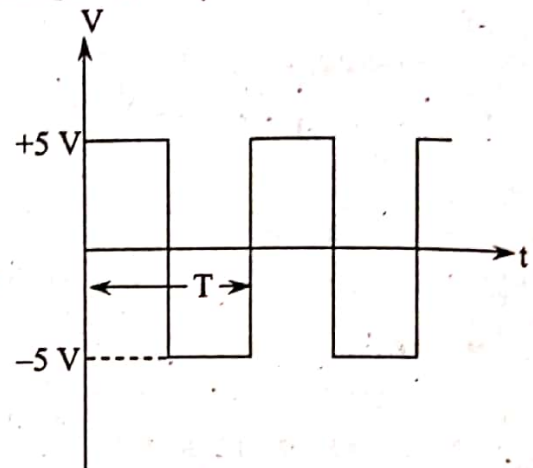


Figure (1)

The output voltage levels of high pass filter are  $V_1$ ,  $V_1'$ ,  $V_2$  and  $V_2'$ .

The steady state maximum output voltage is,  $V_1'$  and is given as,

$$V_1' = V_1 e^{-T/RC} \quad \dots (1)$$

The steady state minimum output voltage is,  $V_2'$  and is given as,

$$V_2' = V_2 e^{-T/RC} \quad \dots (2)$$

To find out the values of  $V_1'$  and  $V_2'$ , first calculate the value of  $V_1$  and  $V_2$ . By using the equations,  $V_2 = -V_1$ ,  $V_1 = V_2' = V$  and  $V_2' = -V_1'$ , we can write,

$$V_1 = \frac{V}{1 + e^{-T/RC}} = \frac{10}{1 + e^{-0.002/1 \times 10^{-3}}} = 8.8$$

$$\therefore V_1 = 8.8 \text{ volts}$$

Substitute the value of  $V_1$  in equation (1), we get,

$$V_1' = V_1 e^{-T/RC} = 8.8(e^{-2 \times 10^{-3}/1 \times 10^{-3}}) = 1.19$$

$$\therefore V_1' = 1.19 \text{ volts}$$

Similarly, we have,

$$V_1' - V_2 = V$$

$$\therefore V_2 = \frac{-V e^{-T/RC}}{1 + e^{-T/RC}} = \frac{-1.35}{1 + 0.135} = -1.189$$

$$\therefore V_2 = -1.189$$



Substitute the value of ' $V_2'$ ' in equation (2), we get,

$$\begin{aligned} V_2' &= V_2 e^{-T_2/RC} \\ &= (-1.189)(e^{-2 \times 10^{-3}/1 \times 10^{-3}}) \\ &= (-1.189)(0.135) \\ &= -0.16 \end{aligned}$$

$$\therefore V_2' = -0.16 \text{ volts}$$

$\therefore$  Therefore, the output voltage levels under steady state are,

$$\begin{aligned} V_1 &= 8.8 \text{ volts} \\ V_1' &= 1.19 \text{ volts} \\ V_2 &= -1.189 \text{ volts} \\ V_2' &= -0.16 \text{ volts.} \end{aligned}$$

The output waveform is shown in figure (2).

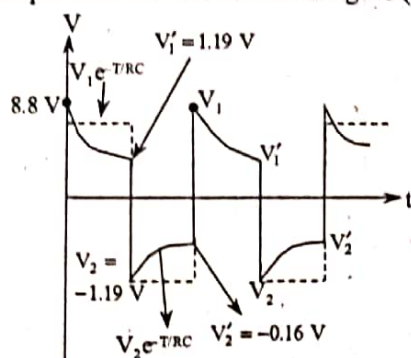


Figure (2)

Q40. A square wave whose peak-to-peak value is 1 V extends  $\pm 0.5$  V with reference to ground. The half period is 0.1 sec. This voltage impressed upon an RC differentiating circuit whose time constant is 0.2 sec. Determine the maximum and minimum values of output voltage in the steady state.

Ans: Given that,

Peak to peak amplitude of input is  $V = 1$  V and extends  $\pm 0.5$  V with respect to ground.

The positive duration is  $T_1 = 0.1$  sec

The negative duration is  $T_2 = 0.2$  sec

The time constant  $RC, \tau = 0.2$  sec

Figure (a) illustrates the input waveform applied to the high-pass RC circuit.

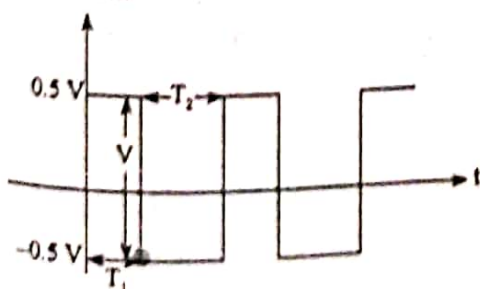


Figure (a)

From the data, the time constant  $RC$  is comparable with  $T_1$  and  $T_2$ .

Since the shape of the output of a high-pass RC circuit for square wave input (any input) depends on time constant, the output waveform is as illustrated in figure (b).

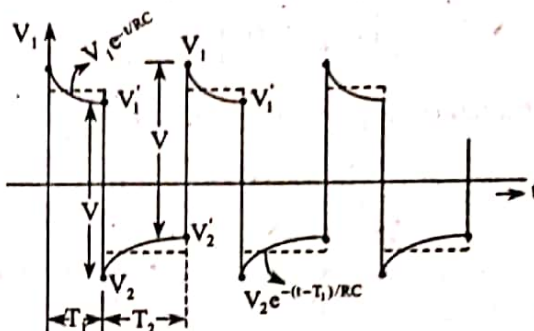


Figure (b): Output Waveform of RC High-pass Circuit for Square Wave Input

From figure (b),

$$V_1' = V_1 e^{-T_1/RC} \quad \dots (1)$$

$$V_2' = V_2 e^{-T_2/RC} \quad \dots (2)$$

The steady state maximum value of output is  $V_1'$  and

The steady state minimum value of output is  $V_2'$

$\therefore$  To calculate  $V_1'$  and  $V_2'$  we have to calculate  $V_1$  and  $V_2$  as  $V$  extends equally as  $\pm 0.5$  with respect to ground we have,

$$V_1 = -V_2 \quad \dots (3)$$

$$\text{Also, } V_1 - V_2' = V \quad \dots (4)$$

Substituting equations (2) and (3) in equation (4), we get,

$$V_1 + V_1 e^{-T_2/RC} = V$$

$$\Rightarrow V_1 = \frac{V}{1 + e^{-T_2/RC}}$$

$$\Rightarrow V_1 = \frac{1}{1 + e^{-0.2/0.2}} = 0.7310$$

$$\Rightarrow V_1' = V_1 e^{-T_1/RC}$$

$$\Rightarrow V_1' = 0.7310 e^{-0.1/0.2}$$

$$\Rightarrow V_1' = 0.443$$

Similarly we have,

$$V_1' - V_2' = V$$

$$\Rightarrow \frac{V_1}{e^{-T_1/RC}} - V_2 = V$$

$$\Rightarrow \frac{-V_2}{e^{-T_1/RC}} - V_2 = V$$

$$\therefore V_2 = \frac{-V e^{-T_1/RC}}{1 + e^{-T_1/RC}} \quad \dots (5)$$

We have,  $V'_2 = V_2 e^{-T_2/RC}$

Substituting equation (5) in  $V'_2$ , we get,

$$V'_2 = \frac{(-V e^{-T_1/RC})(e^{-T_2/RC})}{(1 + e^{-T_1/RC})}$$


$$\Rightarrow V'_2 = \frac{-V e^{-(T_1+T_2)/RC}}{(1 + e^{-T_1/RC})}$$

$$\Rightarrow V'_2 = \frac{-1 e^{-(0.3)/0.2}}{1 + e^{-0.1/0.2}} = \frac{-0.223}{1.606}$$

$$\therefore V'_2 = -0.1388$$

$\therefore$  The steady state maximum and minimum values of the output of high-pass RC circuit for square wave input are  $V'_1 = 0.443$  V and  $V'_2 = -0.1388$  respectively.

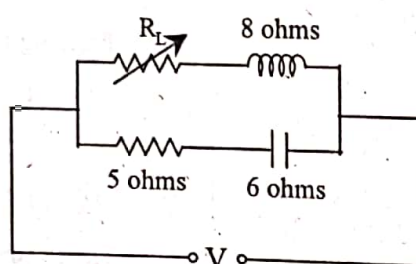**Q41.** Draw the locus diagram and obtain the value of  $R_L$  in the circuit shown in below figure which results in resonance for the circuit.




Figure

**Ans:**

**Note:** In the given problem the value of the source voltage is not specified. Hence assume it to be 230 V (r.m.s).  
The given circuit is shown in figure.

Model Paper-II, Q5(a)

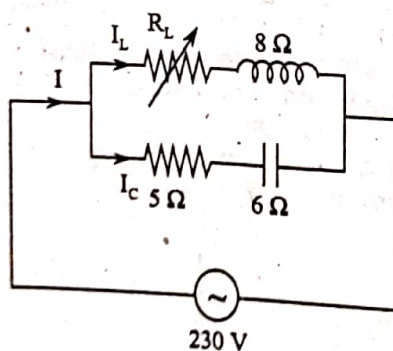

Figure

Now,

Impedance of branch-1,

$$Z_C = R_C - jX_C$$

$$= 5 - j6$$

$$= 7.81 \angle -50.19^\circ$$

Current through branch-1,

$$I_C = \frac{V}{Z_C}$$

$$= \frac{230 \angle 0^\circ}{7.81 \angle -50.19^\circ}$$

$$= 29.45 \angle 50.19^\circ \text{ A}$$

The branch current  $I_c$  is of fixed magnitude equal to 29.45 A and leads the applied voltage by  $50.19^\circ$ .

Now,

Impedance of branch-2,

$$\begin{aligned} Z_L &= R_L + jX_L \\ &= R_L + j8 \end{aligned}$$

When,  $R_L = 0$

$$\begin{aligned} Z_L &= j8 \\ &= 8 \angle 90^\circ \end{aligned}$$

$\therefore$  Current through branch-2

$$\begin{aligned} I_L &= \frac{V}{Z_L} \\ &= \frac{230 \angle 0^\circ}{8 \angle 90^\circ} \\ &= 28.75 \angle 90^\circ \end{aligned}$$

$$\therefore I_L = 28.75 \angle 90^\circ \text{ A}$$

The current  $I_L$  lags behind the applied voltage by  $90^\circ$ .

As  $R_L$  increases,  $Z_L$  increase and hence  $I_L$  decreases.

The locus of the current  $I_L$  is a semi-circle lying below the voltage phasor, since  $I_L$  lags behind the voltage.

Also the diameter of the semicircle is = 28.75 A

#### Steps to Draw Locus Diagram

1. Take the applied voltage  $V = 230$  V the reference phasor on x-axis.
2. Take a scale of 1 cm = 4 A on the y-axis.
3. Draw  $I_L = OA = 28.75$  A = 7.2 cm on the negative y-axis since  $I_L$  lags  $V$  by  $90^\circ$ .
4. With midpoint  $B$  of  $OA$  draw the semicircle.
5. Now, draw  $I_c = OC = 29.45$  A = 7.36 cm at an angle  $\phi = 50.19$  with respect to the applied voltage.
6. Draw  $CD$  parallel to  $OA$  and magnitude equal to  $OA$ .
7. With centre  $E$ , the midpoint of  $CD$  draw the semicircle.
8. Consider a point 'F' on the semicircle arbitrarily such that  $CF = OG = I_L$ .
9. Join  $CF$ ,  $OF$  and  $FG$ .
10. Measure  $OF$  from the locus diagram.  
Thus  $OF = I = 8.5$  cm =  $8.5 \times 4 = 34$  A
11. Now from triangle  $OFC$ ,

$$\begin{aligned} FC &= \sqrt{OF^2 - OC^2} \\ &= \sqrt{34^2 - 29.45^2} \\ &= \sqrt{288.7} \\ &= 16.99 \\ &\approx 17 \text{ A} \end{aligned}$$

$$12. \quad FC = I_L = 17 \text{ A}$$

$$\text{But, } I_L = \frac{V}{Z_L}$$

$$\Rightarrow I_L = \frac{V}{\sqrt{R^2 + X_L^2}}$$

$$\Rightarrow 17 = \frac{230}{\sqrt{R^2 + 8^2}}$$

$$\Rightarrow \sqrt{R^2 + 8^2} = \frac{230}{17}$$







## For Capacitor

The maximum energy stored in capacitor =  $\frac{1}{2} CV^2$

Energy released per cycle =  $P \times T$

$$= \frac{V^2}{2 \times R} \times \frac{1}{f}$$

$$= \frac{V^2}{2Rf}$$

$$\therefore \text{Quality factor, } Q = \frac{2\pi \times \frac{1}{2} CV^2}{\frac{V^2}{2Rf}}$$

$$= \frac{2\pi CV^2}{2} \times \frac{2Rf}{V^2}$$

$$= \omega CR$$

$$\therefore Q = \omega CR$$

**Q48.** A parallel circuit has two branches, branch 1 has a resistance of  $5 \Omega$  connected in series with an inductance  $10 \text{ mH}$ . A capacitor is connected in branch 2, the parallel circuit is connected across a  $230 \text{ V}$ ,  $50 \text{ Hz}$  supply. If the circuit is to be in resonance, find the value of the capacitance. Find the current drawn from the supply and also find the currents in branches (1) and (2).

**Ans:**

Given that,

Resistance of branch 1,  $R = 5 \Omega$

Inductance of branch 1,  $L = 10 \text{ mH} = 0.01$

Supply voltage,  $V = 230 \text{ V}$

Frequency,  $f = 50 \text{ Hz}$

According to given data, the circuit obtained is as shown in figure (a).

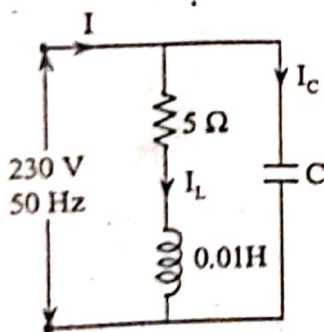


Figure (a)

Let,  $Y_1$ ,  $Y_2$  be the admittances of the two parallel branches.

Let,  $X_C$  be the capacitive reactance of the capacitor and  $X_L$  be the inductive reactance of the inductor.

$$\begin{aligned} X_L &= 2\pi fL \\ &= 2 \times \pi \times 50 \times 0.01 \\ &= 3.14 \Omega \end{aligned}$$

$$Y_1 = \frac{1}{5 + j3.14}$$

$$Y_2 = \frac{1}{-jX_C}$$

The total admittance is given by,

$$\begin{aligned} Y &= Y_1 + Y_2 \\ &= \frac{1}{5 + j3.14} + \frac{1}{-jX_C} \end{aligned} \quad \dots (1)$$

Rationalizing the denominators of equation (1),

$$\begin{aligned} Y &= \frac{1}{5 + j3.14} \times \frac{5 - j3.14}{5 - j3.14} + \frac{1}{-jX_C} \cdot \frac{jX_C}{jX_C} \\ &= \frac{5 - j3.14}{34.86} + \frac{j}{X_C} \end{aligned}$$

Separating the real and imaginary parts,

$$Y = \left( \frac{5}{34.86} \right) + j \left[ \frac{1}{X_C} - \frac{3.14}{34.86} \right]$$

For the circuit to be at resonance, the imaginary part of admittance must be zero.

$$\text{i.e., } \frac{1}{X_C} - \frac{3.14}{34.86} = 0$$

$$\Rightarrow \frac{1}{X_C} = \frac{3.14}{34.86}$$

$$\Rightarrow X_C = 11.10 \Omega$$

We know that, the capacitive reactance is given by,

$$X_C = \frac{1}{2\pi fC}$$

Capacitance,

$$\begin{aligned} C &= \frac{1}{2\pi f X_C} \\ &= \frac{1}{2\pi \times 50 \times 11.10} \\ &= 286 \mu\text{F} \end{aligned}$$

Current through branch 1 is given by,

$$\begin{aligned} I_1 &= \frac{V}{Z_1} \\ &= \frac{230 \angle 0^\circ}{5 + j3.14} = \frac{230 \angle 0^\circ}{5.90 \angle 32.12^\circ} \\ &= 38.98 \angle -32.12^\circ \text{ A} \end{aligned}$$

Current through branch 2 is given by,

$$\begin{aligned} I_2 &= \frac{V}{Z_2} = \frac{V}{X_C} \\ &= \frac{250}{11.10} \\ &= 22.52 \text{ A} \end{aligned}$$

Under resonance condition, the imaginary part will be zero, hence only the real part exists i.e., only the active component. Therefore, total current taken from the supply under resonance condition is given by,

$$\begin{aligned} I &= I_L \cos \phi \\ &= 38.98 \cos (32.12^\circ) \\ &= 33.01 \text{ A} \end{aligned}$$


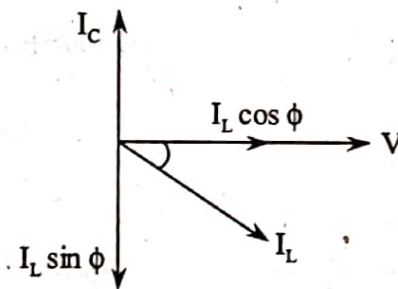


Figure (b)

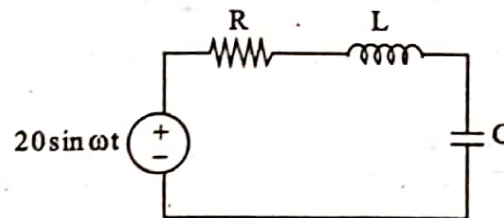Q49. In the circuit shown in below figure,  $R = 2 \text{ ohms}$ ,  $L = 1 \text{ mH}$  and  $C = 0.4 \text{ } \mu\text{F}$ .

- Find the resonant frequency and the half-power frequencies.
- Calculate the quality factor and bandwidth.
- Determine the amplitude of the currents at resonant and half-power frequencies  $\omega_0$ ,  $\omega_1$ , and  $\omega_2$ .



Figure

Model Paper-III, Q4(b)

Given that,

$$R = 2 \text{ } \Omega$$

$$L = 1 \text{ mH}$$

$$C = 0.4 \text{ } \mu\text{F}$$

The given circuit diagram is shown in figure (1),

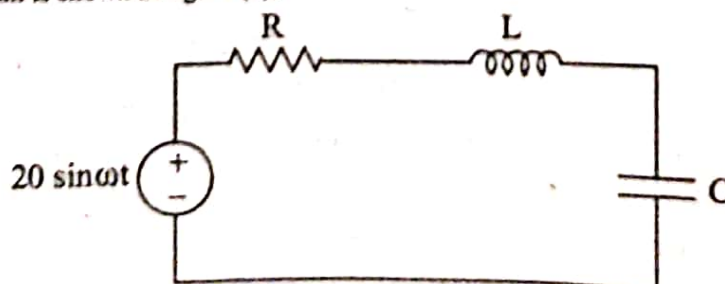


Figure (1)



To determine,

- (a) (i) Resonant frequency,  $\omega_0 = ?$   
 (ii) Half-power frequencies,  $\omega_1 = ?$  and  $\omega_2 = ?$   
 (b) (i) Quality factor,  $Q = ?$   
 (ii) Bandwidth,  $B = ?$   
 (c) Amplitude of current at,  
 $\omega = \omega_0, \omega_1, \omega_2 = ?$

(a)

(i) Resonant frequency,  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$= \frac{1}{\sqrt{1 \times 10^{-3} \times 0.4 \times 10^{-6}}}$$

$$= \frac{1}{2 \times 10^{-5}}$$

$$= 50 \text{ k rad/sec}$$

(ii) Half-power frequencies

We know that,

The lower half-power frequency is given as,

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$= -\frac{2}{2 \times (1 \times 10^{-3})} + \sqrt{\left[\frac{2}{2 \times (1 \times 10^{-3})}\right]^2 + \left[\frac{1}{(1 \times 10^{-3}) \times (0.4 \times 10^{-6})}\right]}$$

$$= -1000 + \sqrt{(1000)^2 + 25 \times 10^8}$$

$$= 49009.999 \text{ rad/sec}$$

$$= 49.009 \text{ k rad/sec}$$

And also,

The upper half-power frequency is given as,

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$= \frac{2}{2 \times (1 \times 10^{-3})} + \sqrt{\left[\frac{2}{2 \times (1 \times 10^{-3})}\right]^2 + \left[\frac{1}{(1 \times 10^{-3}) \times (0.4 \times 10^{-6})}\right]}$$

$$= 1000 + \sqrt{(1000)^2 + 25 \times 10^8}$$

$$= 51009.999 \text{ rad/sec}$$

$$= 51.009 \text{ k rad/sec}$$

(b)

(i) Quality factor,  $Q = \frac{\omega_0 L}{R}$

$$= \frac{50 \times 10^3 \times (1 \times 10^{-3})}{2}$$

$$= \frac{50 \times 10^3 \times 10^{-3}}{2} = \frac{50}{2} = 25$$

(ii) Bandwidth,  $B = \frac{R}{L} = \frac{2}{(1 \times 10^{-3})}$   
 $= 2 \times 10^3 \text{ rad/sec}$   
 $= 2 \text{ k rad/sec}$

(c) Amplitude of current

At resonating frequency, the amplitude of current is given as,

$$I = \frac{V_m}{R}$$

$$= \frac{20}{2} \quad [\because V = V_m \sin \omega t = 20 \sin \omega t]$$

$$[\because V_m = 20]$$

$$I = 10 \text{ A}$$

At half-power frequencies (i.e.,  $\omega = \omega_1 = \omega_2$ ), the amplitude of current is given as,


$$I = \frac{V_m}{\sqrt{2}R} = \frac{20}{\sqrt{2} \times 2} = \frac{10}{\sqrt{2}}$$

$$I = 7.07106 \text{ A}$$

Result

- (a) (i) Resonant frequency,  $\omega_0 = 50 \text{ k rad/sec}$   
 (ii) Half-power frequencies,  $\omega_1 = 49.009 \text{ k rad/sec}$   
 $\omega_2 = 51.009 \text{ k rad/sec}$
- (b) (i) Quality factor,  $Q = 25$   
 (ii) Bandwidth,  $B = 2 \text{ k rad/sec}$
- (c) Amplitude of current,  
 At  $\omega = \omega_0$ ,  $I = 10 \text{ A}$   
 At  $\omega = \omega_1, \omega_2$ ,  $I = 7.07106 \text{ A}$

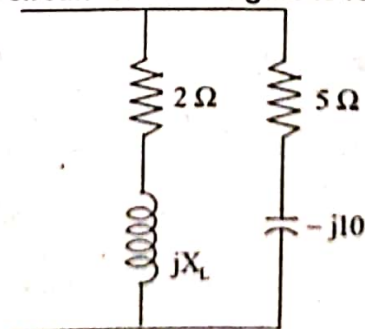
Q50. Find the value of 'L' for which the circuit shown in figure is resonant at a frequency of  $\omega = 500 \text{ rad/s}$ .



Figure

Ans:

The given circuit is,

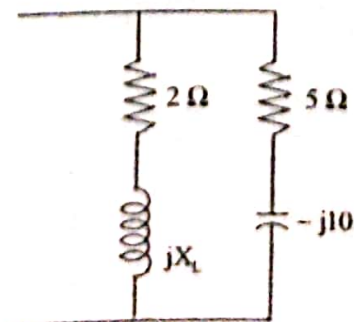

Figure



To determine,

The value of inductance ( $L$ ) at resonant frequency,  $\omega = 500$  rad/sec. From figure, the total admittance of the circuit is given

as,

$$\begin{aligned}
 Y_r &= Y_L + Y_C \\
 \Rightarrow Y_r &= \frac{1}{Z_L} + \frac{1}{Z_C} \\
 \Rightarrow Y_r &= \frac{1}{2 + jX_L} + \frac{1}{5 - j10} \\
 \Rightarrow Y_r &= \frac{1}{2 + jX_L} \times \frac{(2 - jX_L)}{(2 - jX_L)} + \frac{1}{5 - j10} \times \frac{(5 + j10)}{(5 + j10)} \\
 \Rightarrow Y_r &= \frac{(2 - jX_L)}{2^2 - (jX_L)^2} + \frac{(5 + j10)}{5^2 - (j10)^2} \\
 \Rightarrow Y_r &= \frac{2 - jX_L}{4 + X_L^2} + \frac{5 + j10}{25 + 100} \\
 \Rightarrow Y_r &= \frac{2}{4 + X_L^2} - j \frac{X_L}{4 + X_L^2} + \frac{5}{125} + j \frac{10}{125} \\
 Y_r &= \frac{2}{4 + X_L^2} - j \frac{X_L}{4 + X_L^2} + \frac{1}{25} + j \frac{2}{25} \\
 \therefore Y_r &= \left[ \frac{2}{4 + X_L^2} + \frac{1}{25} \right] + j \left[ \frac{2}{25} - \frac{X_L}{4 + X_L^2} \right] \quad \dots (1)
 \end{aligned}$$

Now, under resonance condition, the imaginary term in equation (1) becomes zero.

$$\Rightarrow \frac{2}{25} - \frac{X_L}{4 + X_L^2} = 0$$

$$\frac{2}{25} = \frac{X_L}{4 + X_L^2}$$

$$8 + 2X_L^2 = 25X_L$$

$$\Rightarrow 2X_L^2 - 25X_L + 8 = 0$$

On solving the above quadratic equation, we get,

$$X_L = 12.17 \, \Omega \text{ and } X_L = 0.33 \, \Omega$$

But,

$$X_L = \omega L$$

$$\Rightarrow L = \frac{X_L}{\omega_0}$$

Where,

$$X_L = 12.17 \, \Omega, \text{ then,}$$

$$L = \frac{12.17}{500}$$

$$= 0.024 \, \text{H}$$

$$= 24.34 \, \text{mH}$$

$$\text{If } X_L = 0.33 \, \Omega$$

$$L = \frac{0.33}{500}$$

$$= 0.00066 \, \text{H}$$

$$= 0.66 \, \text{mH}$$

$$\therefore L = 24.34 \, \text{mH or } 0.66 \, \text{mH}$$