

① Draw block diagrams of following

a. AM low level and high level transmitters

b. FM direct and indirect transmitter

c. Radio receivers

i. TRF receiver

ii. Superhetrodyne receiver

d. superhetrodyne tracking

e. Padder, Trimmer and S point tracking along with respective graphs.

f. IF Amplifiers.


g. Simple and practical diode detector diagrams.

h. Amplitude limiter diagram along with Amplitude limiter characteristics and typical response characteristics.

i. FM superhetrodyne receiver.


Ans:

a) AM Low-Level Transmitter :-

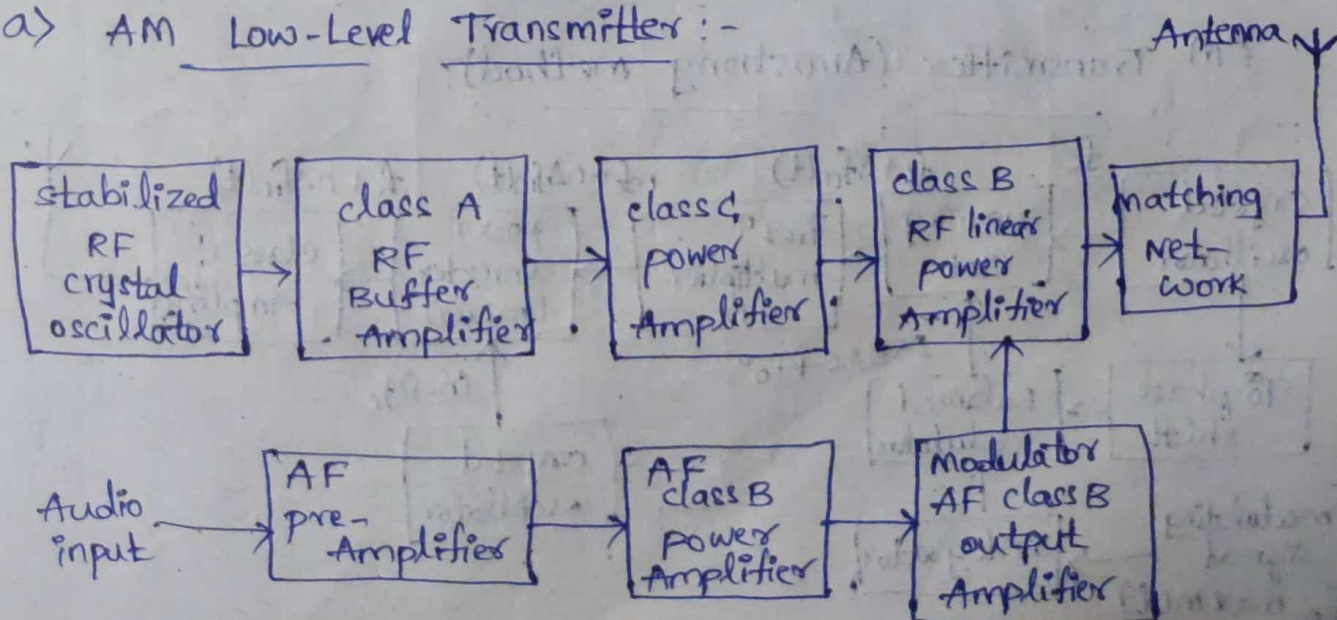


## ② AM High-Level Transmitter:-

Antenna

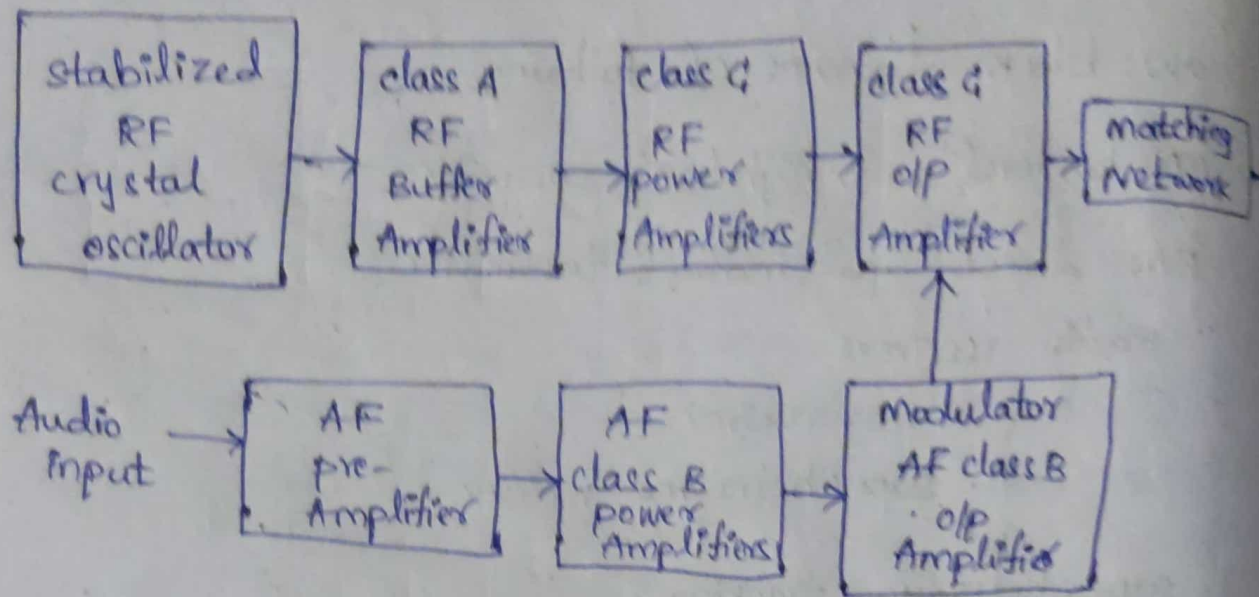


b)
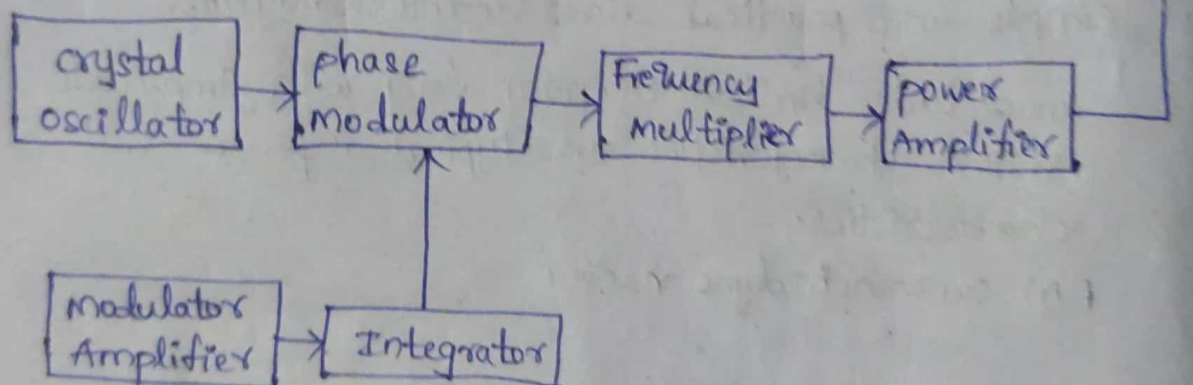
## Indirect (phase) modulated FM Transmitter:




## FM Transmitter (Armstrong method):

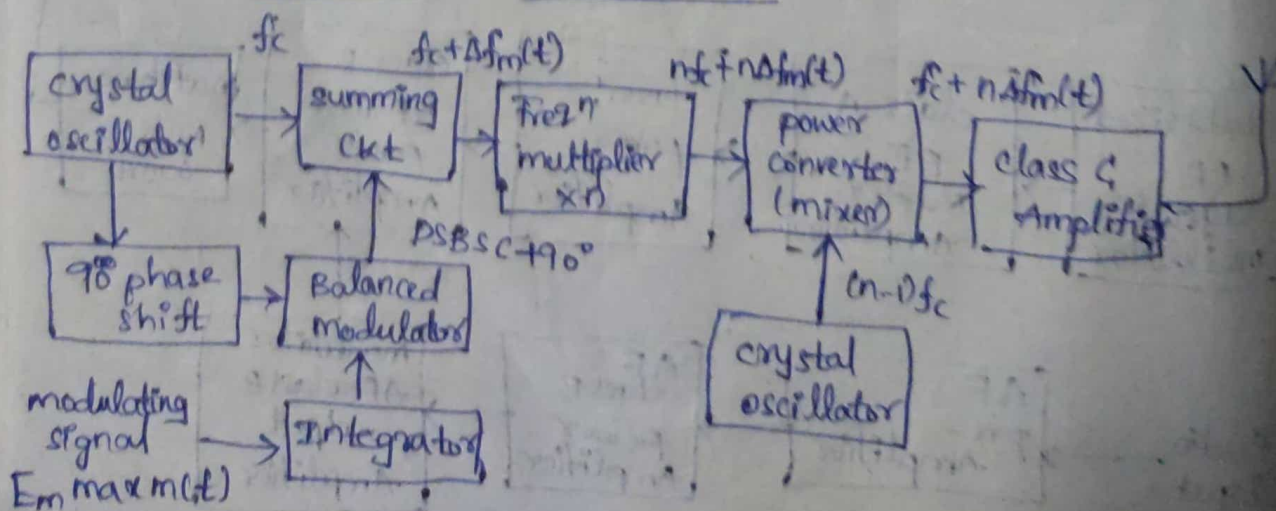





### B) TRF Receiver:

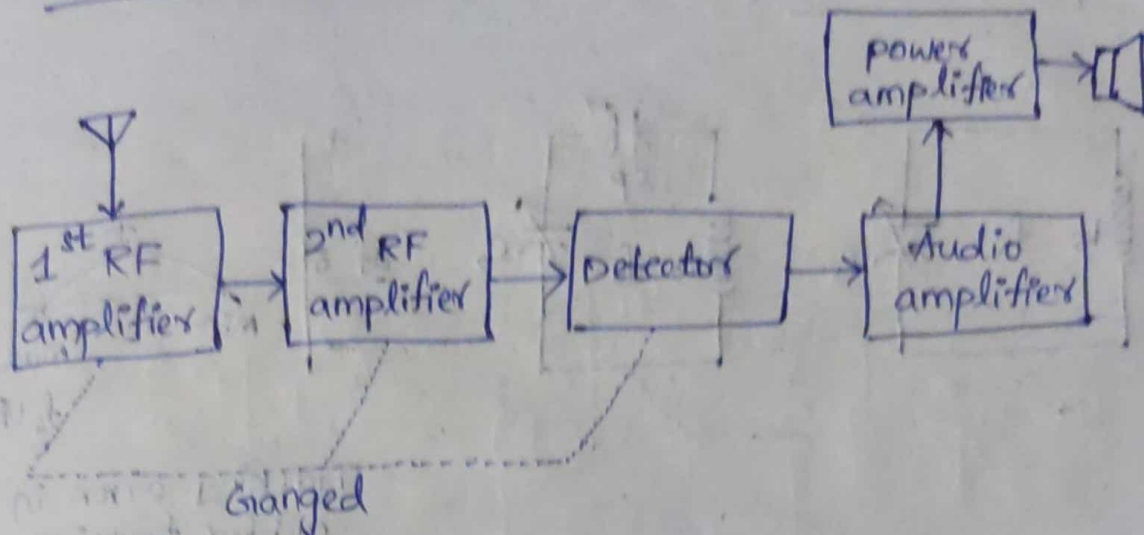

### superhetrodyne Receiver :-

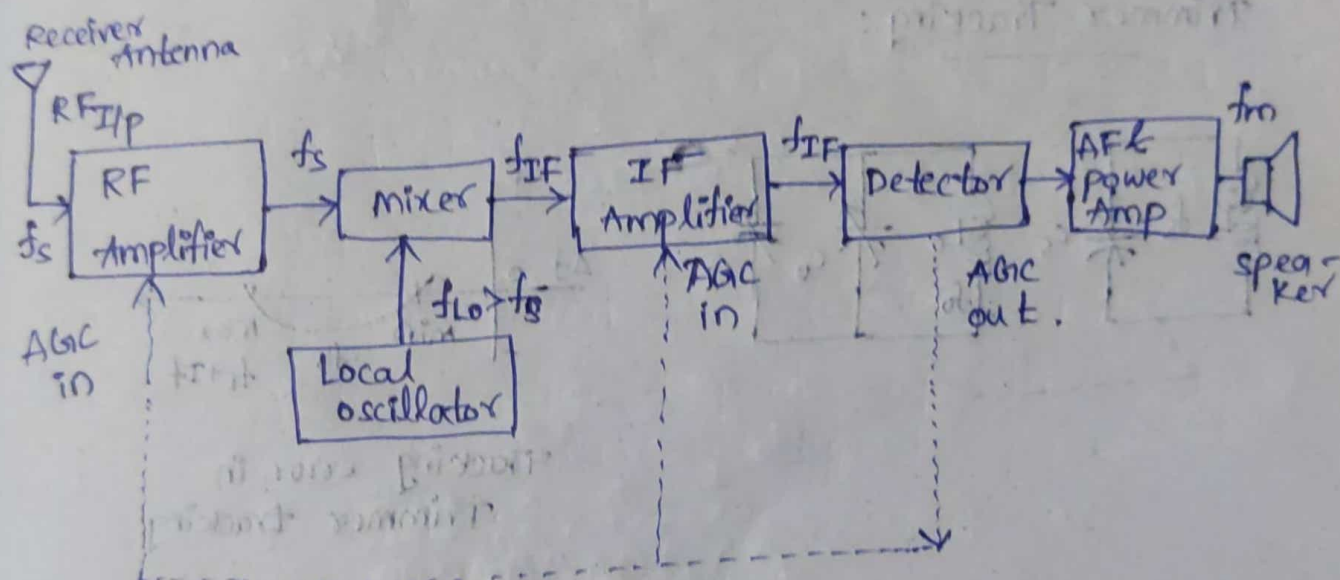


### d) superheterodyne Tracking :-

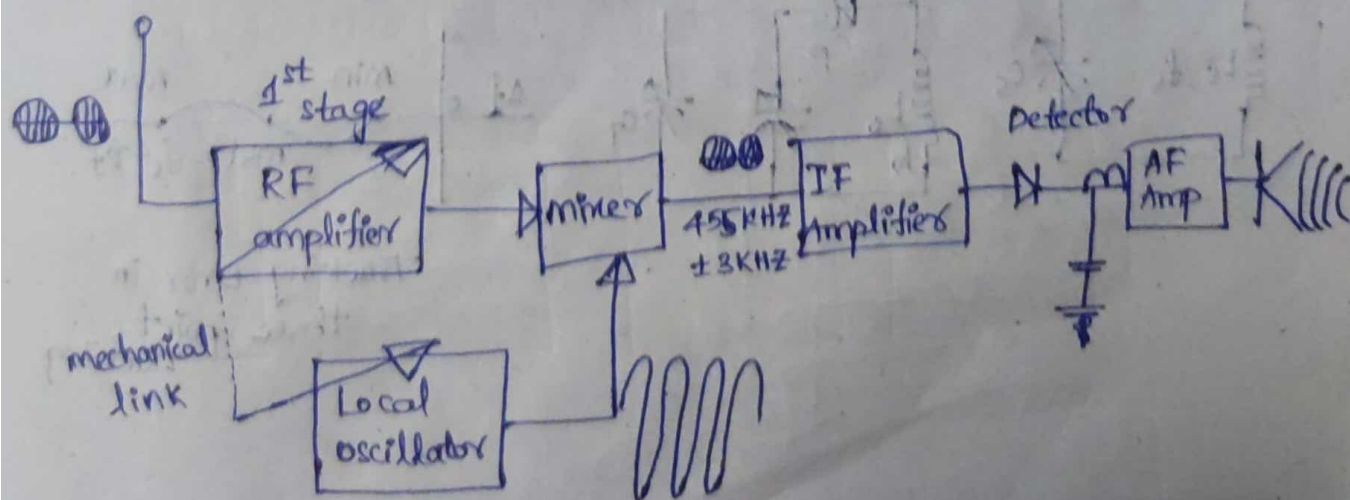


④

### e) Padder Tracking:-

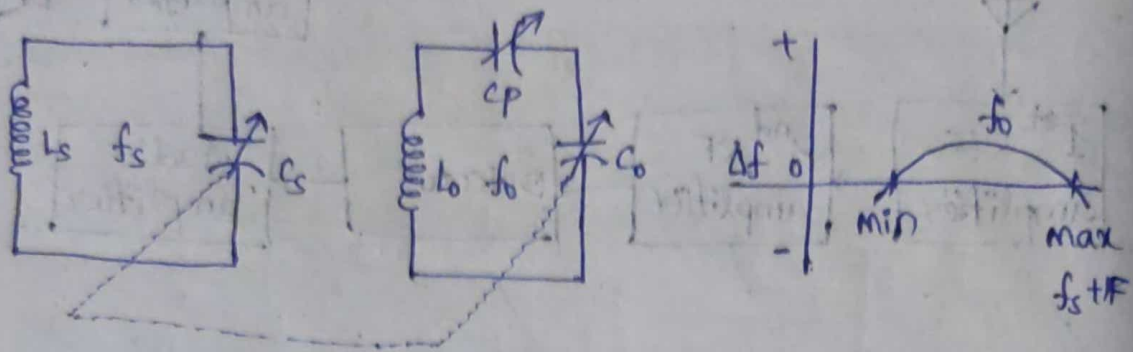


Tracking error in  
padder tracking

### Trimmer Tracking:

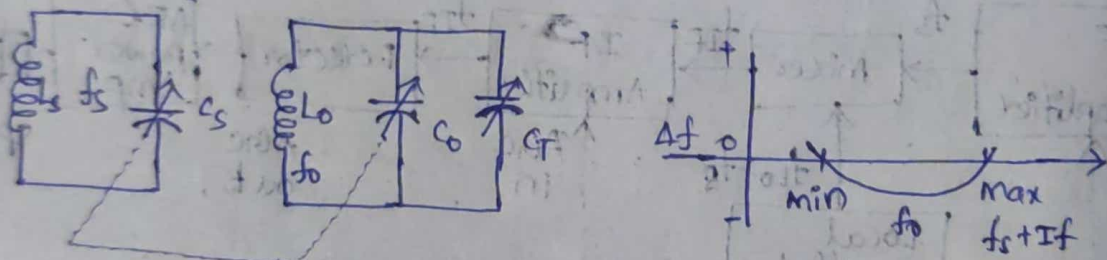


Tracking error in  
Trimmer tracking

### Three point Tracking:

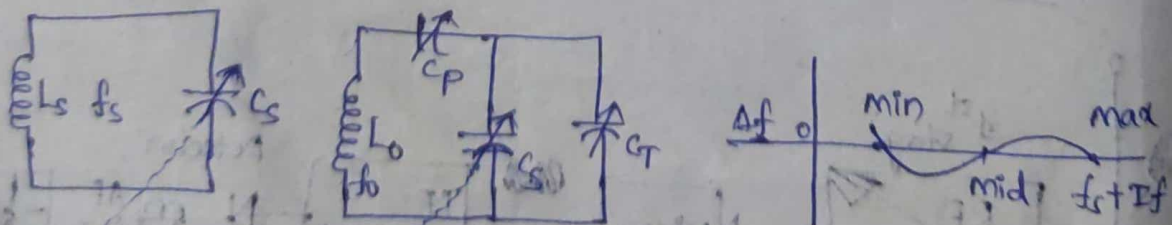


Tracking Error in  
three point tracking


### ③ f) IF Amplifiers (FET)

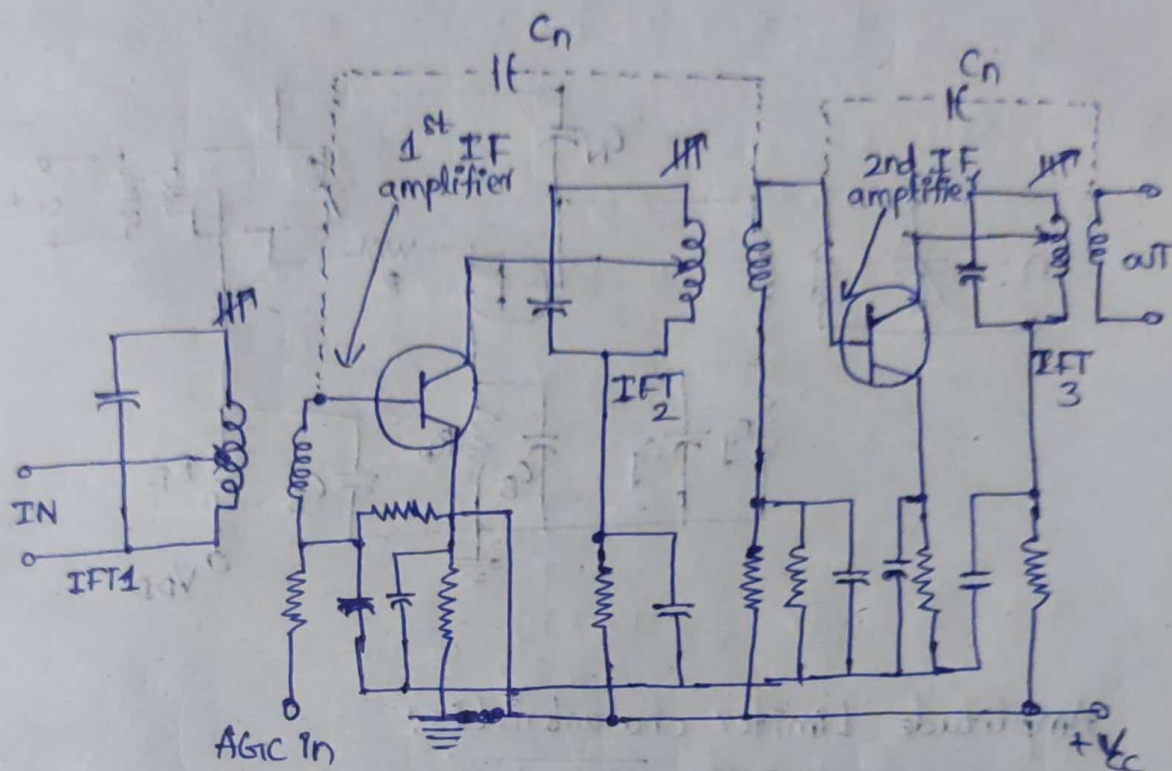

### g) simple Diode Detector :-

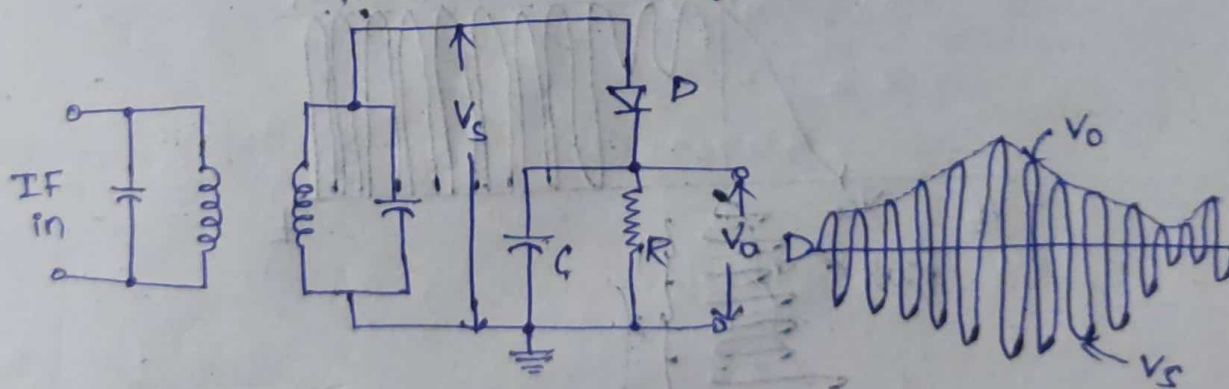


### Practical Diode Detector:

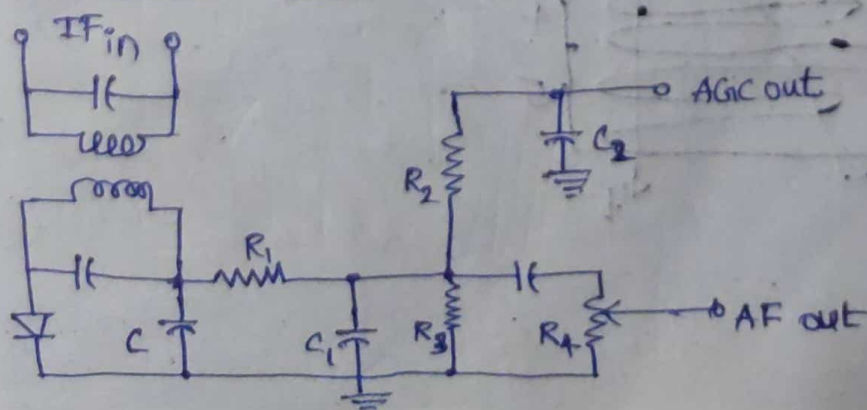




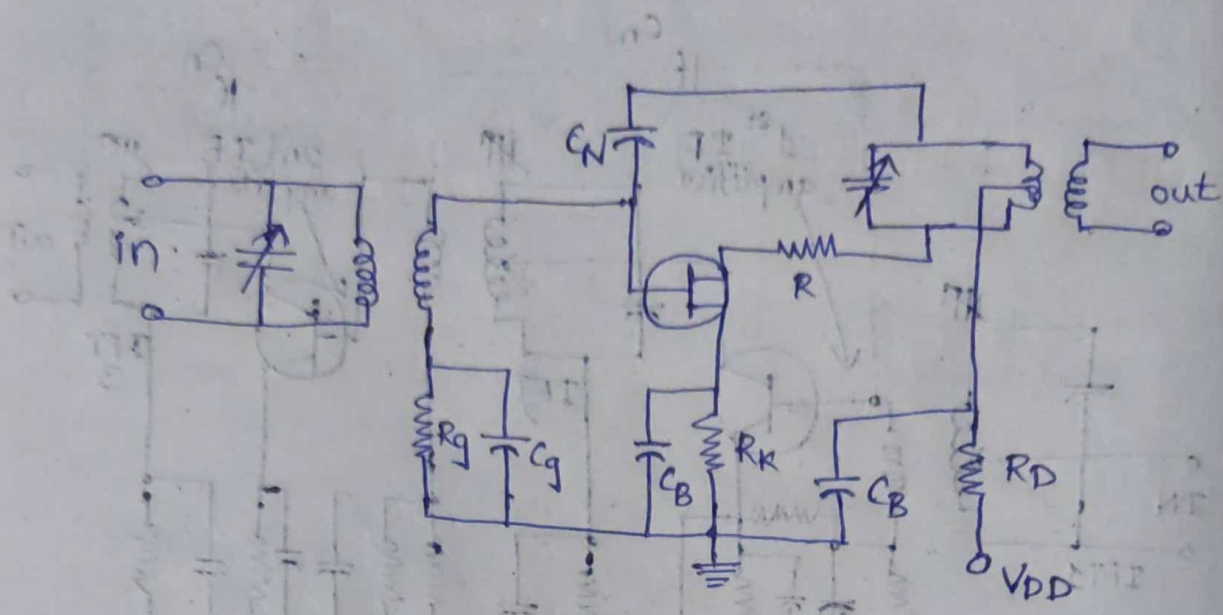
⑥ h) Simple Amplitude Limiter CKT (using FET):




Amplitude Limiter characteristics:

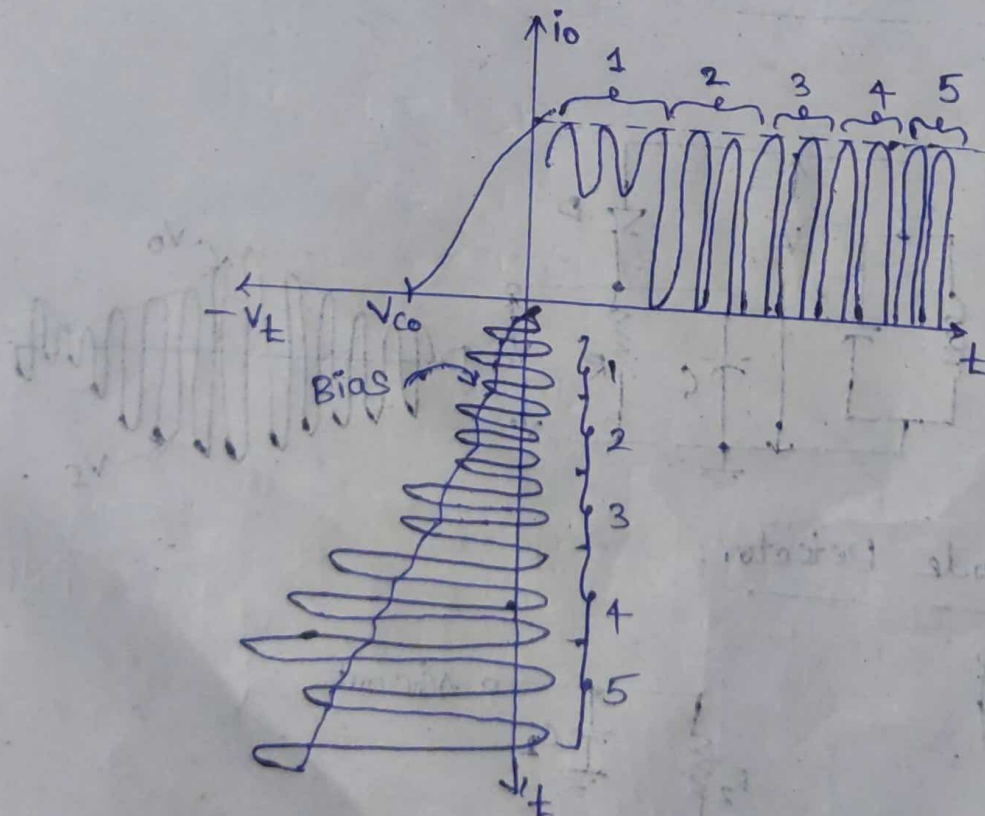

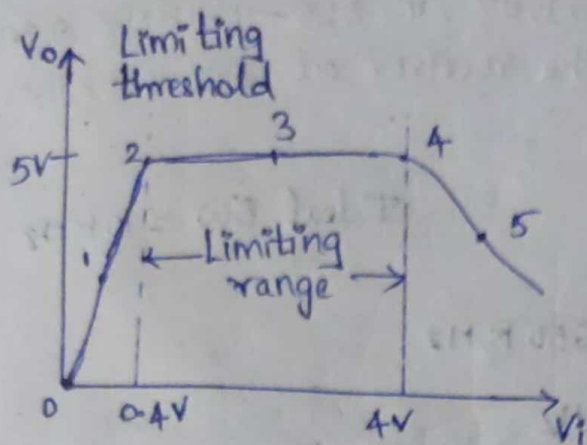⑦ typical Limiter response characteristics:



i) FM superheterodyne Receiver:

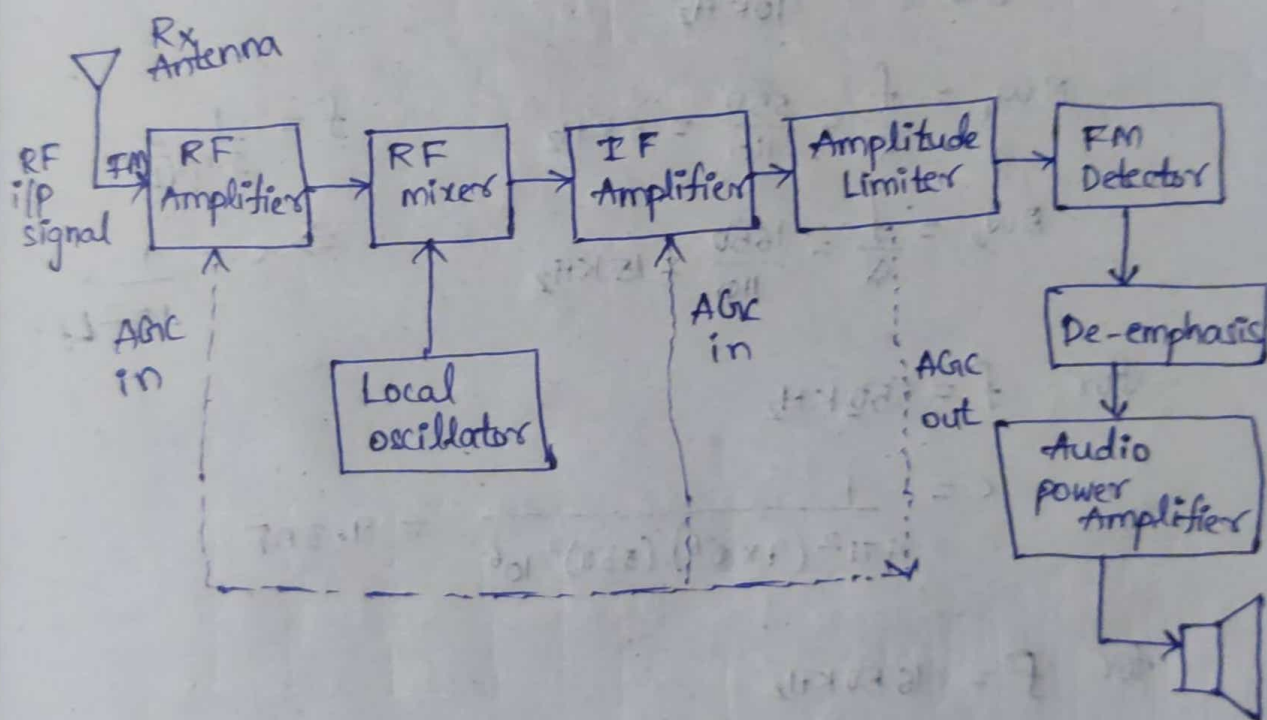

- ② A TRF Receiver is to be designed with single tuned ckt using  $9\mu\text{H}$  inductor. The capacitance range of the variable capacitance in LC Tank ckt require to tune the receiver in  $550-1650\text{KHz}$  range, calculate the B.W of the receiver at  $550-1650\text{KHz}$ .

Sol: Given,

$$L = 9\mu\text{H}$$

$$\text{Ideal BW} = 10\text{KHz}$$

$$f_r = 550 \text{ to } 1650\text{KHz}$$

$$f_r = 1100\text{KHz}$$

$$C = ?$$

$$\text{Bandwidth} = ?$$

$$Q = \frac{f_r}{\text{BW}} = \frac{1100\text{KHz}}{10\text{KHz}} = 110$$

$$\text{BW}_1 = \frac{f}{Q} = \frac{550}{110} = 5\text{KHz}$$

$$\text{BW}_2 = \frac{f}{Q} = \frac{1650}{110} = 15\text{KHz}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow C = \frac{1}{4\pi^2 L f^2}$$

$$\text{for } f = 550\text{KHz}$$

$$C = \frac{1}{4\pi^2 (9 \times 10^{-6}) (550 \times 10^3)^2} = 9.3\text{nF}$$

$$\text{for } f = 1650\text{KHz}$$

$$C = \frac{1}{4\pi^2 (9 \times 10^{-6}) (1650 \times 10^3)^2} = 1.03\text{nF}$$



⑨ ③ calculate Q.F of LC tuned ckt having resonant frequency of 2MHz with internal resistance of coil 60ohms and capacitance value is 50pF.

sol!

Given,

$$f_r = 2\text{MHz}$$

$$R = 60\Omega$$

$$C = 50\text{pF}$$

$$Q.F = ?$$

$$Q = \frac{f_r}{\text{BW}} \quad (\text{or}) \quad R = \frac{X_L}{Q} \Rightarrow Q = \frac{X_L}{R}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow L = \frac{1}{4\pi^2 f_r^2 C} = \frac{1}{4\pi^2 \times 4 \times 10^{12} \times 50 \times 10^{-12}}$$

$$= \frac{1}{16 \times \pi^2 \times 50}$$
$$= 126.6\mu\text{H}$$

$$Q = \frac{X_L}{R} = \frac{2\pi f_r L}{R}$$
$$= \frac{2\pi \times 2 \times 10^6 \times 126.6 \times 10^{-6}}{60}$$
$$= \frac{4\pi \times 126.6}{60}$$
$$= 26.51$$

$$\therefore \text{Quality factor} = 26.51$$

- ⑤<sup>10</sup> In a broad cast superheterodyne receiver, having no RF amplifier, the loaded QF of antenna coupling ckt is 50. If the image frequency is 2MHz and IF is 455KHz. calculate the signal frequency and IFRR.

Sol:

given,

$$QF = 50$$

$$f_{si} = 2 \times 10^6 \text{ Hz}$$

$$IF = 455 \times 10^3 \text{ Hz}$$

$$f_s = ? \quad IFRR = ?$$

$$f_{si} = f_s + 2IF$$

$$\Rightarrow f_s = (-2IF + f_{si})$$

$$= 2 \times 10^6 - 2(455 \times 10^3)$$

$$= 2 \times 10^3 (10^3 - 455)$$

$$= 1090 \text{ KHz}$$

$$P = \frac{f_{si}}{f_s} = \frac{f_s}{f_{si}}$$

$$= \frac{2 \times 10^6}{1090 \times 10^3} = \frac{1090 \times 10^3}{2 \times 10^6}$$

$$= \frac{200}{109} = \frac{109}{200} = 1.29$$

$$\therefore P = 1.29$$

$$X = \sqrt{P^2 Q^2 + 1} = \sqrt{(1.29)^2 (50)^2 + 1}$$

$$= 64.4$$

$$\therefore \underline{\underline{f_s = 1090 \text{ KHz}}}, \underline{\underline{IFRR = 64.4}}$$



(11)

- ④ A tuned ckt is having a  $20\mu\text{H}$  coil connected in parallel with a  $100\text{pF}$  capacitor. Calculate the desired coil resistances for  $200\text{kHz}$  BW

Sol:Given,  $L = 20\mu\text{H}$ 

$$C = 100\text{pF}$$

$$\text{BW} = 200\text{kHz}$$

$$R = ?$$

$$R = \frac{X_L}{Q} = \frac{2\pi f L}{f} \times \text{BW}$$

$$= 2\pi L \text{BW}$$

$$R = 2\pi L \text{BW}$$

$$= 2\pi \times 20 \times 10^{-6} \times 200 \times 10^3$$

$$= 8 \times \pi \times 10^{-6} \times 10^6$$

$$= 8 \times \pi$$

$$= 25.13\Omega$$

$$\therefore \boxed{R = 25.1\Omega}$$

- ⑥ A broadcast superheterodyne receiver, has IF  $455\text{kHz}$  and it is tuned to  $1500\text{kHz}$ . Calculate the IF and QF of tuned ckt having  $\text{IRR} = 75$ .

Sol:

Given,

$$\text{IF} = 455\text{kHz}$$

$$f_s = 1500\text{kHz} = 1.5\text{MHz}$$

$$\text{IRR} = 75$$

$$\text{IF} = ? \quad \text{QF} = ?$$

12

$$\begin{aligned}
 f_{SI} &= f_s + 2IF \\
 &= 1500 + 2(455) \\
 &= 1500 + 910 \\
 &= 2410 \text{ KHz} \\
 &= 2.41 \text{ MHz}
 \end{aligned}$$

$$p = \frac{f_{SI}}{f_s} - \frac{f_s}{f_{SI}} = \frac{2.41}{1.5} - \frac{1.5}{2.41} = 0.98$$

$$\alpha = \sqrt{p^2 Q^2 + 1}$$

$$\Rightarrow Q = \sqrt{\frac{\alpha^2 - 1}{p^2}} = \sqrt{\frac{(95)^2 - 1}{(0.98)^2}}$$

$$= \sqrt{\frac{5624}{(0.98)^2}}$$

$$= \sqrt{5835.8}$$

$$= 76.5$$

$$\therefore QF = 76.5 \rightarrow f_{SI} = 2.41 \text{ MHz}$$

⑦ when a superheterodyne receiver is tuned to 555 <sup>kHz</sup> Its LO provides the mixer with a input at 1010 KHz. what is the IF? If the antenna of this receiver is connected to mixer via a tuned ckt whose load Q is 40. what will be the rejection ratio of calculated IF.



(3)

soln

Given,

$$f_s = 555 \text{ KHz}$$

$$f_i = 1010 \text{ KHz}$$

$$Q = 40, \text{ IF} = ?, \alpha = ?$$

$$\begin{aligned} \text{I.F} &= f_i - f_s \\ &= 1010 - 555 \\ &= 455 \text{ KHz} \end{aligned}$$

$$\begin{aligned} f_{si} &= f_s + 2 \cdot \text{I.F} \\ &= 555 + 2(455) \\ &= 910 + 555 \\ &= 1465 \text{ KHz} \end{aligned}$$

$$\alpha = \sqrt{p^2 Q^2 + 1}$$

$$\begin{aligned} p &= \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}} \\ &= \frac{1465}{555} - \frac{555}{1465} \\ &= 2.63 - 0.37 \\ &= 2.26 \end{aligned}$$

$$p = 2.26$$

$$\begin{aligned} \alpha &= \sqrt{(40)^2 (2.26)^2 + 1} \\ &= \sqrt{1600 (5.1) + 1} \\ &= 90.3 \end{aligned}$$

$$\therefore \boxed{\alpha = 90.3}$$

$$\therefore \text{IF} = 455 \text{ KHz}$$

$$\alpha = \underline{\underline{90.3}}$$

- ② In a broadcast superheterodyne receiver, having no RF amplifier, the loaded QF of antenna coupling (kt) is 100. If the IF used is 455 KHz, calculate the image frequency. calculate the IRR at 1000 KHz.

(14)

Sol:

Given,

$$Q = 100$$

$$IF = 455 \text{ KHz}$$

$$\text{at } f_s = 1000 \text{ KHz}$$

$$IRR = ? \quad f_{si} = ?$$

$$f_{si} = 1000 + 2(455)$$

$$= 1910 \text{ KHz}$$

$$IRR = \sqrt{f^2 Q^2 + 1}$$

$$f = \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}}$$

$$= \frac{1910}{1000} - \frac{1000}{1910}$$

$$= 1.910 - 0.523$$

$$= 1.387$$

$$IRR = \sqrt{(1.387)^2 (100)^2 + 1}$$

$$= \sqrt{1.92 (10000) + 1}$$

$$= 138.7$$

$$\therefore f_{si} = 1910 \text{ KHz}$$

$$IRR = 138.7$$



5

- ② calculate the IRR of receiver having RF amplifier with IF of 450 KHz. If D.F of relevant coil are 65 at incoming frequency of 1200 KHz and 20 MHz.

Ans: Given,

$$IF = 450 \text{ KHz} = 0.45 \text{ MHz}$$

$$Q = 65$$

$$f_{si} = 1200 \text{ KHz}$$

$$f_{s2} = 20 \text{ MHz}$$

$$IRR = ?$$

Formulas:-

$$IRR = \sqrt{p^2 Q^2 + 1}$$

$$p = \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}}$$

$$f_{si} = f_s + 2IF$$

$$\triangleright f_s = 1200 \text{ KHz}$$

$$f_{si} = f_s + 2IF$$

$$= 1200 + 2(450)$$

$$= 2100 \text{ KHz}$$

$$p = \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}} = \frac{2100}{1200} - \frac{1200}{2100}$$

$$= 1.17$$

$$\alpha = \sqrt{1 + (65)^2 (1.17)^2} = \sqrt{578 + 26}$$

$$= 76.05$$

$$\therefore \alpha_1 = 76.05$$

$$\alpha_2 = 5.29$$

$$\text{ii) } f_s = 20 \times 10^6 \text{ Hz}$$

$$= 20 \text{ MHz}$$

$$f_{si} = 20 + 2(0.45)$$

$$= 20.9 \text{ MHz}$$

$$p = \frac{20.9}{20} - \frac{20}{20.9}$$

$$= 0.08$$

$$\alpha = \sqrt{(0.08)^2 (65)^2 + 1}$$

$$= \sqrt{28.04}$$

$$= 5.29$$

- 10) The RF Lo freq and IF of AM receiver are  $800 \text{ KHz}$ ,  $1255 \text{ KHz}$ ,  $455 \text{ KHz}$  respectively. Determine image freq, IRR for a loaded  $Q$  of 120.

Sol: Given,

$$f_L = 1255 \text{ KHz}$$

$$\text{IF} = 455 \text{ KHz}$$

$$Q = 120$$

$$f_s = 800 \text{ KHz}$$

$$\begin{aligned} f_{si} &= f_s + 2\text{IF} \\ &= 800 + 2(455) \\ &= 1710 \text{ KHz} \end{aligned}$$

$$\text{IRR} = \sqrt{p^2 Q^2 + 1}$$

$$\begin{aligned} p &= \frac{1710}{800} - \frac{800}{1710} \\ &= 2.13 - 0.46 \end{aligned}$$

$$p = 1.67$$

$$\begin{aligned} \text{IRR} &= \sqrt{(2.78)(120)^2 + 1} \\ &= \sqrt{14400(2.78) + 1} \\ &= 200.08 \end{aligned}$$

$$\therefore \boxed{\text{IRR} = 200.08}$$



- ⑪ For a receiver with IF, & F & Lo Freq of 455 KHz, 1100 KHz, 1555 KHz respectively. Determine image frequency, IRR for a loaded Q of 50. (17)

Soln-

given,

$$IF = 455 \text{ KHz}$$

$$f_s = 1100 \text{ KHz}$$

$$f_l = 155 \text{ KHz}$$

$$Q = 50$$

$$f_{si} = ? \quad IRR = ?$$

$$f_{si} = f_s + 2 * IF$$

$$f_{si} = 1100 + 2(455) = 1100 + 910 \\ = 2010 \text{ KHz}$$

$$f = \frac{2010}{1100} - \frac{1100}{2010} = 1.82 - 0.54 \\ = 1.28$$

$$IRR = \sqrt{(0.28)^2 (50)^2 + 1} \\ = \sqrt{1.63(2500) + 1} \\ = \sqrt{4076} \\ = 63.84$$

$$\therefore f_{si} = 2010 \text{ KHz}$$

$$IRR = \underline{\underline{63.84}}$$